

# Hardware Design with VHDL

## An Introduction (created by Ronald Hecht)

Henning Puttnies and Eike Schweißguth

University of Rostock  
Institute of Applied Microelectronics and Computer Engineering

October 17, 2016

# Outline

- 1 Introduction
- 2 VHDL for Synthesis
- 3 Simulation with VHDL
- 4 Frequent Mistakes
- 5 Advanced Concepts

# Outline

- 1 Introduction
- 2 VHDL for Synthesis
- 3 Simulation with VHDL
- 4 Frequent Mistakes
- 5 Advanced Concepts


# What are HDLs?

- Modeling language for electronic designs and systems
- VHDL, Verilog
- PALASM, ABEL
- Net list languages such as EDIF, XNF
- Test languages such as e, Vera
- SystemC for hardware/software co-design and verification

# HDL for ...

- Formal description of hardware
- Specification on all abstraction layers
- Simulation of designs and whole systems
- Design entry for synthesis
- Standard interface between CAD tools
- Design reuse

# Design methodology

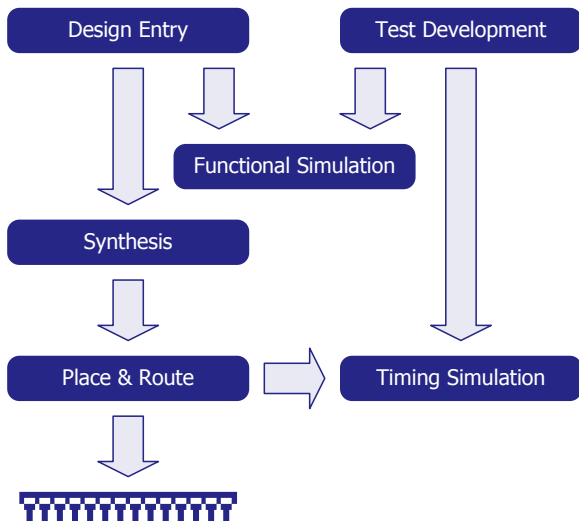

# Pros and Cons of HDLs


## Pros

- Speeds up the whole design process
- Powerful tools
- Acts as an interface between tools
- Standardized
- Design reuse

## Cons

- Learning curve
- Limited support for target architecture

# Design Abstraction Levels

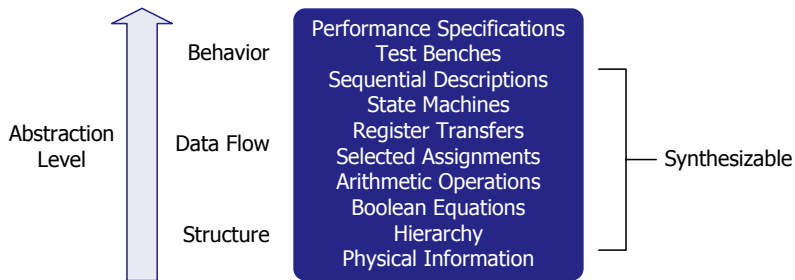


**Behavior** Sequential statements, implicit registers

**Data flow** Register transfer level (RTL), Parallel statements, explicit registers

**Structure** Design hierarchy, Wiring components

# HDL Abstraction Levels

 

# Outline

- 1 Introduction
- 2 VHDL for Synthesis**
- 3 Simulation with VHDL
- 4 Frequent Mistakes
- 5 Advanced Concepts


# A First Example

## Multiplexer

```
library ieee ;
use ieee . std_logic_1164 . all ;

entity mux is
  port (
    a, b : in   std_logic_vector (3 downto 0);
    s    : in   std_logic ;
    o    : out  std_logic_vector (3 downto 0));
end mux;

 architecture behavior of mux is
begin -- behavior
  o <= a when s = '0' else b;
end behavior;
```



# Library

```
library ieee ;  
use ieee . std_logic_1164 . all ;
```

- Makes library ieee visible
- Use objects within the library
- Use package std\_logic\_1164
- Makes std\_logic and std\_logic\_vector visible

# Entity

```
entity mux is  
  port (  
    a, b : in   std_logic_vector (3 downto 0);  
    s    : in   std_logic ;  
    o    : out  std_logic_vector (3 downto 0));  
end mux;
```

- Defines the name of the module
- Describes the interface
  - Name of the ports
  - Direction
  - Type

# Architecture


```
architecture behavior of mux is  
begin  -- behavior  
    o <= a when s = '0' else b;  
end behavior;
```

- Implements the module
  - Behavior
  - Structure
  - RTL description
- Entity and architecture are linked by name (mux)
- Name of architecture (behavior)
- More than one architecture per entity allowed

# Parallel Processing
 
## Half Adder

```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity half_adder is  
  port (  
    a, b : in std_logic;  
    s, co : out std_logic);  
end half_adder;  
  
architecture rtl of half_adder is  
begin -- rtl  
  s <= a xor b;  
  co <= a and b;  
end rtl;
```




- Implicit gates
- Signals are used to wire gates
- Computes signals  $s$  and  $co$  from  $a$  and  $b$  in **parallel**
 
## Full Adder

```
entity full_adder is
  port (
    a, b, ci : in  std_logic ;
    s, co   : out std_logic );
end full_adder ;
```

```
architecture beh_par of full_adder is
  signal s1, s2, c1, c2 : std_logic ;
begin -- behavior
  -- half adder 1
  s1 <= a xor b;
  c1 <= a and b;
  -- half adder 2
  s2 <= s1 xor ci;
  c2 <= s1 and ci;
  -- evaluate s and co
  s <= s2;
  co <= c1 or c2;
end beh_par;
```



- All statements are processed in **parallel**
- A signal **must not** be driven at two places
- Order of statements is irrelevant

# Sequential Processing – Processes

```
architecture beh_seq of full_adder is
begin  -- beh_seq

    add: process (a, b, ci)
        variable s_tmp, c_tmp : std_logic ;
    begin  -- process add
        -- half adder 1
        s_tmp := a xor b;
        c_tmp := a and b;
        -- half adder 2
        c_tmp := c_tmp or (s_tmp and ci);
        s_tmp := s_tmp xor ci;
        -- drive signals
        s <= s_tmp;
        co <= c_tmp;
    end process add;

end beh_seq;
```

- All statements are processed sequential
- Sensitivity list (a, b, ci)
- Multiple variable assignments are allowed
- Order of statements is relevant
- Variables are updated immediately
- Signals are updated at the end of a process
- Try to avoid multiple signal assignments

# Parallel versus Sequential Processing


```
p1: process (a, b)
begin  -- process p1
      -- sequential statements
      -- ...
      -- drive process outputs
      x <= ...
end process p1;

p2: process (c, x)
begin  -- process p2
      -- sequential statements
      -- ...
      -- drive process outputs
      y <= ...
end process p2;

-- drive module outputs
o <= x or y;
```

- process p1, process p2 and o are processed in parallel
- Statements within processes are sequential
- Inter-process communication with signals
- Signal values are evaluated recursively in zero time
- Simulator uses delta cycles

# Real time and delta cycles

 

# Signals and Variables

## Signals


- Inside and outside processes
- Communication between parallel statements and processes
- Only the last assignment within a process is evaluated
- Signal is updated at the end of a process
- Signals are wires

## Variables

- Inside processes only
- For intermediate results
- Multiple assignments allowed
- Immediate update
 
# Structural Description

- Module composition
- Wiring of Modules
- Design Hierarchy
- “Divide and conquer”



```
architecture structural of full_adder is
  component half_adder
    port (
      a, b : in  std_logic ;
      s, co : out std_logic );
  end component;
  signal s1, c1, c2 : std_logic ;
begin -- structural
  half_adder_1 : half_adder
    port map (
      a => a_in, b => b_in,
      s => s1, co => c1);

  half_adder_2 : half_adder
    port map (
      a => ci, b => s1,
      s => s_out, co => c2);

  co_out <= c1 or c2;

end structural ;
```

- Make module half\_adder known with component declaration
- Module instantiation
- Connect ports and signals


# Register

```
entity reg is
  port (
    d, clk : in  std_logic ;
    q       : out std_logic );
end reg;
```

```
architecture rtl of reg is
begin  -- rtl

  reg: process (clk)
  begin  -- process reg
    if rising_edge (clk) then
      q <= d;
    end if ;
  end process reg;

end rtl ;
```

 

- Sensitivity list only contains the clock
- Assignment on the rising edge of the clock
- Not transparent


# Latch

```
entity latch is
  port (
    d, le : in  std_logic ;
    q      : out std_logic );
end latch ;

architecture rtl of latch is
begin  -- rtl

  latch : process (le, d)
  begin  -- process latch
    if le = '1' then
      q <= d;
    end if ;
  end process latch ;

end rtl ;
```

 


- Sensitivity list contains latch enable and data input
- Assignment during high phase of latch enable
- Transparent

# Register with Asynchronous Reset

```
architecture rtl of reg_aset is  
begin -- rtl
```

```
    reg : process (clk, rst)  
    begin -- process reg  
        if rising_edge (clk) then  
            q <= d;  
        end if;  
        if rst = '0' then  
            q <= '0';  
        end if;  
    end process reg;
```

```
end rtl;
```

 

- Sensitivity list contains clock **and reset**
- Reset statement is the last statement within the process
- Reset has highest priority

# Register with Synchronous Reset

```
architecture rtl of reg_sreset is
begin -- rtl

    reg : process (clk)
    begin -- process reg
        if rising_edge (clk) then
            q <= d;
            if rst = '0' then
                q <= '0';
            end if;
        end if;
    end process reg;

end rtl;
```


- Sensitivity list only contains clock
- Reset statement is the last statement within the clock statement
- Should be used if target architecture supports synchronous resets

# Register with Clock Enable

```
architecture rtl of reg_enable is  
begin -- rtl
```

```
    reg : process (clk, rst)  
    begin -- process reg  
        if rising_edge (clk) then  
            if en = '1' then  
                q <= d;  
            end if;  
        end if;  
        if rst = '0' then  
            q <= '0';  
        end if;  
    end process reg;
```

```
end rtl;
```

 


- Enable statement around signal assignment
- Use this semantic!

# Storage Elements – Summary

- Before you start
  - Register or latch?
  - What kind of reset?
  - Clock enable?
- When you code, be precise
  - Sensitivity list
  - Clock statement
  - Enable semantic
  - Reset order/priority
- Prefer registers with synchronous resets
- Check synthesis results
 
# Register Transfer Level (RTL)

- A Module may consist of
  - Pure combinational elements
  - Storage elements
  - Mixture of combinational and storage elements
- Use RTL for
  - shift registers, counters
  - Finite state machines (FSMs)
  - Complex Modules



## Shift register

```
library ieee ;  
use ieee . std_logic_1164 . all ;  
use ieee . numeric_std . all ;  
  
entity shifter is  
  
  port (  
    clk : in   std_logic ;  
    rst : in   std_logic ;  
    o   : out  std_logic_vector (3 downto 0));  
  
end shifter ;  
  
architecture beh of shifter is  
  
  signal value : unsigned(3 downto 0);
```

- Use `ieee.numeric_std` for VHDL arithmetics
- Always `std_logic` for ports
- Internal signal for register

```
begin  -- beh

  shift : process (clk, rst)
begin  -- process shift

    if rising_edge (clk) then
      value <= value rol 1;
    end if;
    if rst = '0' then
      value <= (others => '0');
    end if;

  end process shift ;

  o <= std_logic_vector (value);

end beh;
```

- Clocked signal assignments are synthesized to registers
- Do not forget to drive the outputs

## Counter

```
library ieee ;
use ieee . std_logic_1164 . all ;
use ieee . numeric_std . all ;

entity counter is

    port (
        clk, rst : in  std_logic ;
        o        : out std_logic_vector (3 downto 0));

end counter;

architecture beh of counter is

    signal value : integer range 0 to 15;
```

```
begin -- beh

count: process (clk, rst)
begin -- process count

    if rising_edge (clk) then
        value <= value + 1;
    end if;
    if rst = '0' then
        value <= 0;
    end if;

end process count;

o <= std_logic_vector (to_unsigned (value, 4));

end beh;
```

## Finite State Machine: OPC

```


library ieee;
use ieee.std_logic_1164.all;

entity opc is
  port (
    i      : in  std_logic;
    o      : out std_logic;
    clk, rst : in  std_logic);
end opc;

architecture rtl of opc is

  type state_type is (even, odd);
  signal state : state_type;

```

 

- Declare state types
- Signal for state memory

```
-- State memory and transition logic
trans : process (clk, rst)
begin -- process trans
  if rising_edge (clk) then
    case state is
      when even =>
        if i = '1' then state <= odd;
        end if;
      when odd =>
        if i = '1' then state <= even;
        end if;
    end case;
  end if;
  if rst = '0' then
    state <= even;
  end if;
end process trans;
```

- Transition logic and memory in one process
- Always reset state machines!


```
-- Output logic
output : process (state)
begin -- process output
  case state is
    when even => o <= '0';
    when odd => o <= '1';
  end case;
end process output;

end rtl;
```

- Output logic is placed in a second process
- Unregistered outputs are often problematic

 
# Unregistered Outputs

- Difficult timing analysis
- Combinational loops possible
- Undefined input delay for attached modules
- Glitches


 
# Registered Outputs

- Prefer registered module outputs
- Simplifies the design process
- Prevents glitches and combinational loops



- Exception: Single-cycle handshake
  - Request registered
  - Acknowledge unregistered

# Problems of Traditional RTL Design

## Error-prone

- Many processes and parallel statements
- Many signals
- Accidental latches, multiple signal drivers

## Inflexible Design Patterns


- Combinational logic
- Registers, FSMs

## Schematic-VHDL

- Difficult to understand, to debug, and to maintain
- Focused on the schematic and not on the algorithm
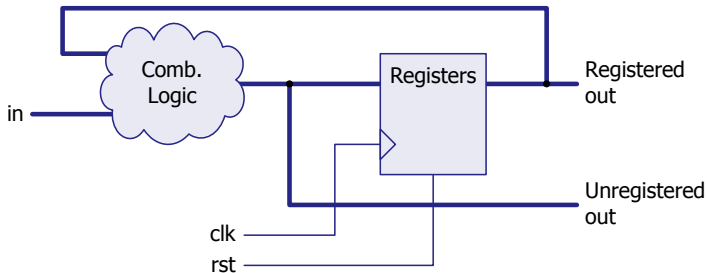
## Solution: Abstracting Digital Logic


- Synchronous designs consist of
  - Combinational logic
  - Registers



- Forget about Moore and Mealy when designing large modules
- They are inflexible and they have unregistered outputs
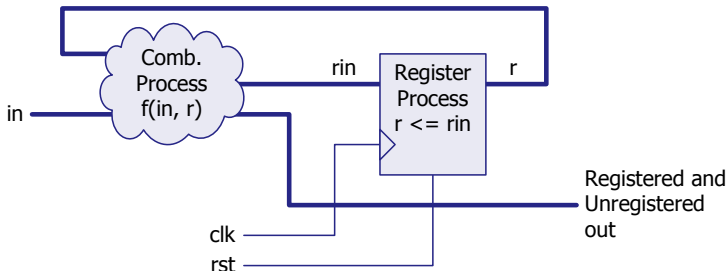
# VHDL Realization

- A module only consists of two processes
  - Combinational process  $rin = f(in, r)$
  - Clocked process  $r = rin$
- Combinational process is sensitive to inputs and registers
- Sequential process is sensitive to clock and reset




# Two-Process Methodology

```

architecture rtl of edge_detect is
  type state_type is (low, high);
  type reg_type is
    record
      state : state_type ;
      o     : std_logic ;
    end record;
  signal r, rin : reg_type;
begin  -- rtl
  reg : process (clk, rst)
  begin  -- process reg
    if rising_edge (clk) then
      r <= rin;
    end if;
    if rst = '0' then
      r.state <= low;
    end if;
  end process reg;

```

 


- Record type for all registers
- Register input rin and output r
- Single process for all registers
- Simplifies adding new registers to the module

```

comb : process (r, i)
  variable v : reg_type;
begin -- process comb
  -- Default assignment
  v := r;
  -- Output is mostly '0'
  v.o := '0';
  -- Finite state machine
  case r.state is
    when low => if i = '1' then
      v.state := high;
      v.o := '1';
    end if;
    when high => if i = '0' then
      v.state := low;
    end if;
  end case;
  -- Drive outputs
  rin <= v;
  o <= r.o;
end process comb;
end rtl;

```

 

- Single process for combinational logic
- Variable  $v$  to evaluate the next register state  $rin$
- Default assignment avoids accidental latches
- Modify  $v$  with respect to  $r$  and inputs
- Assign  $v$  to  $rin$  and drive outputs

# Advantages


## Consistent Coding Style

- Easy to write, to read, and to maintain
- Less error-prone
- High abstraction level
- Concentrates on the algorithm and not on the schematic
- Increases productivity

## Excellent Tool Support

- Fast simulation
- Easy to debug
- Perfect synthesis results

# Debugging

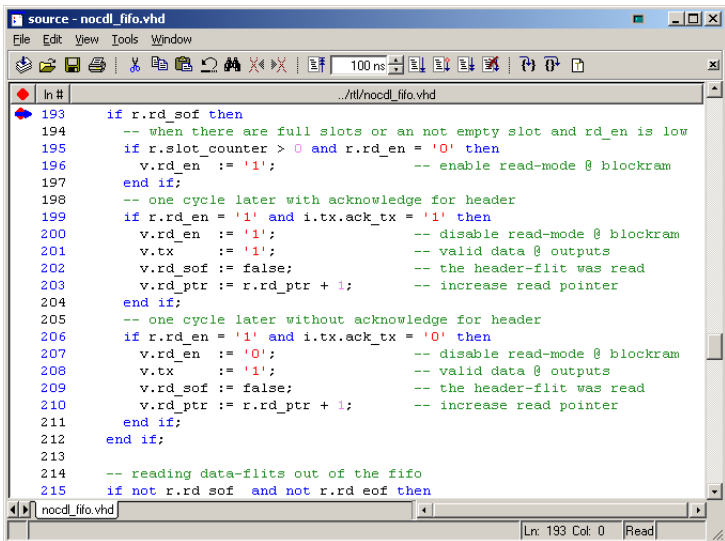

The image shows a screenshot of a text editor window titled "source - nocdl\_fifo.vhd". The window contains VHDL code for a FIFO control logic. The code is as follows:

```
193   if r.rd_sof then
194       -- when there are full slots or an not empty slot and rd_en is low
195       if r.slot_counter > 0 and r.rd_en = '0' then
196           v.rd_en := '1';           -- enable read-mode @ blockram
197       end if;
198       -- one cycle later with acknowledge for header
199       if r.rd_en = '1' and i.tx.ack_tx = '1' then
200           v.rd_en := '1';           -- disable read-mode @ blockram
201           v.tx := '1';             -- valid data @ outputs
202           v.rd_sof := false;       -- the header-flit was read
203           v.rd_ptr := r.rd_ptr + 1; -- increase read pointer
204       end if;
205       -- one cycle later without acknowledge for header
206       if r.rd_en = '1' and i.tx.ack_tx = '0' then
207           v.rd_en := '0';           -- disable read-mode @ blockram
208           v.tx := '1';             -- valid data @ outputs
209           v.rd_sof := false;       -- the header-flit was read
210           v.rd_ptr := r.rd_ptr + 1; -- increase read pointer
211       end if;
212   end if;
213
214   -- reading data-flits out of the fifo
215   if not r.rd_sof and not r.rd_eof then
```

The editor interface includes a menu bar (File, Edit, View, Tools, Window), a toolbar with various icons, and a status bar at the bottom showing "Ln: 193 Col: 0 Read".

# Tips

## Keep the Naming Style

```
signal r, rin : reg_type;  
variable v : reg_type;
```

## Use Default Assignments

```
v.ack := '0';  
if condition then v.ack := '1';  
end if;
```

## Use Variables for Intermediates

```
variable vinc;  
vinc := r.value + 1;
```

## Use Functions and Procedures

```
v.crc := crc_next(r.crc, data, CRC32);  
seven_segment <= int2seg(value);  
full_add(a, b, ci, s, co);
```

## Variables for Unregistered Outs

```
variable v : reg_type  
variable vaddr;  
ack <= v.ack;  
addr <= v.addr;
```

# Design Strategies

## Raise the Abstraction Level!

- Use the two-process methodology
- Use variables
- Use integers, booleans, signed, and unsigned
- Use functions and procedures
- Use synthesizable operators


## Structural Design

- “Divide and Conquer”
- Do not overuse structural design
- But keep the modules testable

# Outline

- 1 Introduction
- 2 VHDL for Synthesis
- 3 Simulation with VHDL**
- 4 Frequent Mistakes
- 5 Advanced Concepts

# Testbench

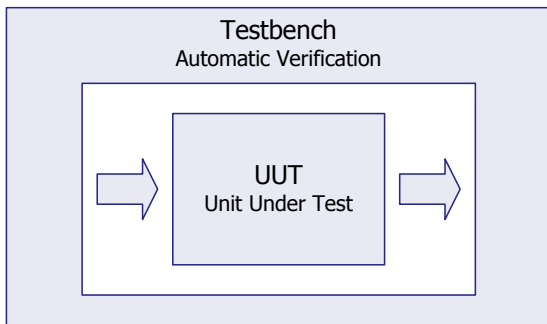

- Testbed for unit under test (UUT), Not synthesizable
- Testbench instantiates UUT
- Generates inputs
- Checks outputs

# A simple VHDL Testbench

```
library ieee ;  
use ieee . std_logic_1164 . all ;  
  
entity half_adder_tb is  
end half_adder_tb ;  
  
architecture behavior of half_adder_tb is  
  
  component half_adder  
    port (  
      a, b : in  std_logic ;  
      s, co : out std_logic );  
  end component ;  
  
  signal a_sig , b_sig  : std_logic ;  
  signal s_sig , co_sig : std_logic ;
```

- Entity is empty
- Declare UUT half\_adder
- Declare signals to interface UUT

```
begin  -- behavior  
  
  -- Unit Under Test  
  UUT: half_adder  
    port map (  
      a => a_sig,  
      b => b_sig,  
      s => s_sig,  
      co => co_sig);
```

- Instantiate UUT
- Connect signals

```
stimuli : process
begin -- process stimuli
  -- generate signals
  a_sig <= '0'; b_sig <= '0';
  wait for 10 ns;
  a_sig <= '1';
  wait for 10 ns;
  a_sig <= '0'; b_sig <= '1';
  wait for 10 ns;
  a_sig <= '1';
  wait for 10 ns;
  -- stop simulation
  wait;
end process stimuli ;

end behavior;
```

- Process to generate test pattern
- No sensitivity list
- Execution until wait statement
- Without wait: Cyclic execution

# Automatic Verification and Bus-functional Procedures

```
library ieee ;
use ieee . std_logic_1164 . all ;
use ieee . numeric_std . all ;
use work . syslog . all ;

entity adder_tb is
  generic (
    -- Adder delay
    period : time := 10 ns);
end adder_tb;

architecture behavior of adder_tb is

  component adder
    port (
      a, b : in  std_logic_vector (3 downto 0);
      sum : out std_logic_vector (3 downto 0);
      co  : out std_logic );
  end component;
```

- Syslog package to generate messages
- Parametrized testbench
- UUT declaration

```
signal a_sig, b_sig : std_logic_vector (3 downto 0)
    := (others => '0');
signal sum_sig : std_logic_vector (3 downto 0);
signal co_sig : std_logic ;
```

```
begin -- behavior
-- Unit Under Test
UUT : adder
    port map (
        a    => a_sig,
        b    => b_sig,
        sum  => sum_sig,
        co   => co_sig);
```

- Declare UUT signals
- Initialize inputs
- Instantiate UUT
- Connect signals

```
-- Stimuli and Verification
```

```
tester : process
```

```
-- Bus-functional procedure for UUT
```

```
procedure add (m, n : in integer range 0 to 15; s : out integer) is
```

```
begin -- do_operation
```

```
    -- set UUT operand inputs
```

```
    a_sig <= std_logic_vector(to_unsigned(m, a_sig'length));
```

```
    b_sig <= std_logic_vector(to_unsigned(n, b_sig'length));
```

```
    -- wait some time
```

```
    wait for period;
```

```
    -- get UUT result
```

```
    s := to_integer(unsigned(co_sig & sum_sig));
```

```
end add;
```

- Bus-functional procedure abstracts UUT interface

**begin**

syslog\_testcase ("Test\_all\_input\_combinations");

**for** i **in** 0 **to** 15 **loop**

syslog(debug, "Operand\_a\_=" &amp; image(i) &amp; " ...");

**for** j **in** 0 **to** 15 **loop**

add(i, j, s);

**if** s /= i + j **then**

syslog(error, "Bad\_result\_for\_" &amp;

image(i) &amp; "\_+\_\_" &amp; image(j) &amp; "\_=" &amp; image(i + j) &amp;

",\_obtained:\_" &amp; image(s));


**end if;****end loop;****end loop;**

syslog\_terminate ;

**end process** tester ;**end behavior;**

- Automatic verification, Debug messages, Termination

# Testing with Reference Models

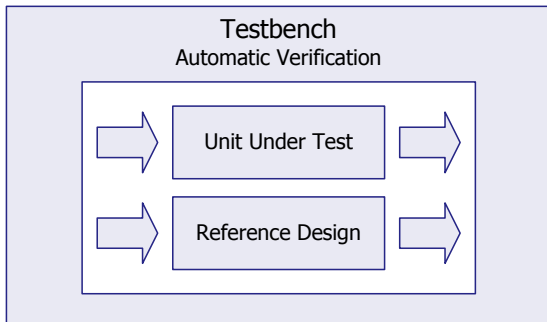


- Instantiate UUT and reference model
- Same test pattern
- Compare results

# Backannotation and Timing Simulation

- Synthesize and place & route UUT
- Backannotate: Extract netlist and timing
- Simulation with testbench
- Use the same testbench as for functional simulation
- **Testbench has to consider real delays**
  - Setup and hold time of registers
  - Pads and wires
- **Never set inputs on clock edge**

# Setup and Hold Time

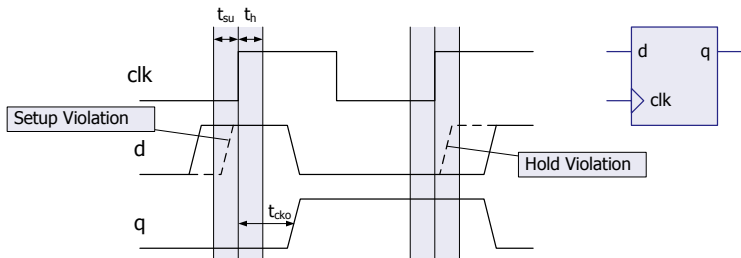

- The setup time  $t_{su}$  defines the time a signal must be stable before the active clock edge
- The hold time  $t_h$  defines the time a signal must be stable after the active clock edge
- The clock-to-out time defines the output delay of the register after the active clock edge
- When setup or hold violation occurs the output is undefined

# Hardware Testbench


- A synthesizable testbench allows to download it into an FPGA
- Examples:
  - Testbench with reference model
  - Build-in self test (BIST)
  - Microprocessor for test pattern generation
- Testbench has ports such as clock, reset and test results
- Very fast
- Considers real wire and logic delays
- Most accurate

# Outline

- 1 Introduction
- 2 VHDL for Synthesis
- 3 Simulation with VHDL
- 4 Frequent Mistakes**
- 5 Advanced Concepts
 
# If statement

```
good_if: process (a, b, sel)
begin -- process good_if
  if sel = '1' then
    o <= a;
  else
    o <= b;
  end if;
end process good_if;
```




- Implements a multiplexer
- This description is optimal

# Cascaded If

```

bad_if: process (a, b, c, d, sel)
begin -- process bad_if
  if sel = "00" then
    o <= a;
  elsif sel = "01" then
    o <= b;
  elsif sel = "10" then
    o <= c;
  else
    o <= d;
  end if;
end process bad_if;


```

 

- Cascaded if statements
- Results in a cascaded multiplexer
- Long delay
 
# Case statement

```
good_case: process (a, b, c, d, sel)
begin -- process bad_if
  case sel is
    when "00" => o <= a;
    when "01" => o <= b;
    when "10" => o <= c;
    when others => o <= d;
  end case;
end process good_case;
```




- Use case statement for multiplexers
- Best synthesis results
 
# Missing sensitivities

```
mux: process (a, b)
begin
  -- process mux
  if sel = '1' then
    o <= a;
  else
    o <= b;
  end if;
end process mux;
```

- Signal sel is missing in sensitivity list
- Process is only activated on a or b
- Simulation error
- Synthesis often correct
- Watch out for synthesis warnings



## Accidental Latches with If Statements

```
if_latch : process (a, b, sel)
begin -- process if_latch
  if sel = "01" then
    o <= a;
  elsif sel = "10" then
    o <= b;
  end if;
end process if_latch ;
```

- Only cases "01" and "10" are covered, other cases missing
- During missing cases o must be stored
- Accidental latch is inferred by synthesis tool
- sel = "01" or sel = "10" acts as latch enable

# Accidental Latches with Case Statements

```
case_latch : process (a, b, c, d, sel)
begin -- process case_latch
  case sel is
    when "00" => o1 <= a;
                o2 <= b;
    when "01" => o1 <= b;
    when "10" => o1 <= c;
                o2 <= a;
    when others => o1 <= d;
                o2 <= c;
  end case;
end process case_latch ;
```

- Assignment for o2 is missing in case sel = "01"
- Accidental latch to store o2

# Circumvent Accidental Latches

```
case_default : process (a, b, c, d, sel )  
begin -- process case_default  
  o1 <= a; o2 <= c;  
  case sel is  
    when "00" => o2 <= b;  
    when "01" => o1 <= b;  
    when "10" => o1 <= c;  
                o2 <= a;  
    when others => o1 <= d;  
  end case;  
end process case_default ;
```

- Use default assignments
- Missing cases are intentional

# Incorrect use of Signals and Variables

```
architecture beh_seq of full_adder is
begin -- beh_seq

    add: process (a, b, ci)
        variable s_tmp, c_tmp : std_logic ;
    begin -- process add
        -- half adder 1
        s_tmp := a xor b;
        c_tmp := a and b;
        -- half adder 2
        c_tmp := c_tmp or (s_tmp and ci);
        s_tmp := s_tmp xor ci;
        -- drive signals
        s <= s_tmp;
        co <= c_tmp;
    end process add;

end beh_seq;
```

- This description is correct
- Do not declare s\_tmp and c\_tmp as signals
- If signals
  - Only last assignment is significant
  - Half adder 1 is removed
  - Combinational loops
- Use signals for wires
- Use variables for combinational intermediate results


# The Package `ieee.numeric_std`

```
library ieee ;  
use ieee . std_logic_1164 . all ;  
use ieee . numeric_std . all ;
```

- Use the package `numeric_std` instead of obsolete `std_logic_signed` and `std_logic_unsigned`
- Avoids ambiguous expressions
- Strict distinction between signed and unsigned vectors
- Sometimes a bit cumbersome but exact

 
# Clocking

- One phase, One clock!
- No clock gating
- Use `rising_edge(clk)`
- Avoid latches, Check synthesis results



 
# Clock scaling

- Scale clock with synchronous counters and enables




 - Use DLLs and PLLs to create other clocks



 
# Asynchronous Signals

- Synchronize asynchronous signals with at least two Registers




 - Prefer registered module outputs – on-chip and off-chip



 
# Resetting

- Do not touch reset without knowledge
- This may cause problems



- Synchronize reset to clock

 

## Other Mistakes

- Use `downto` for all logic vectors

```
std_logic_vector (3 downto 0);
```

- Constrain integers

```
integer range 0 to 7;
```

- Be careful in testbenches with setup and hold time
- Implement signal assignments close to reality

# Not Synthesizable VHDL

- Initializing signals

```
signal q : std logic := '0';
```

- Run-time loops
- Timing specification


```
wait for 10 ns; r <= '1' after 1 ns;
```

- Text I/O
- Floating point

# Outline

- 1 Introduction
- 2 VHDL for Synthesis
- 3 Simulation with VHDL
- 4 Frequent Mistakes
- 5 Advanced Concepts**

# Design Units

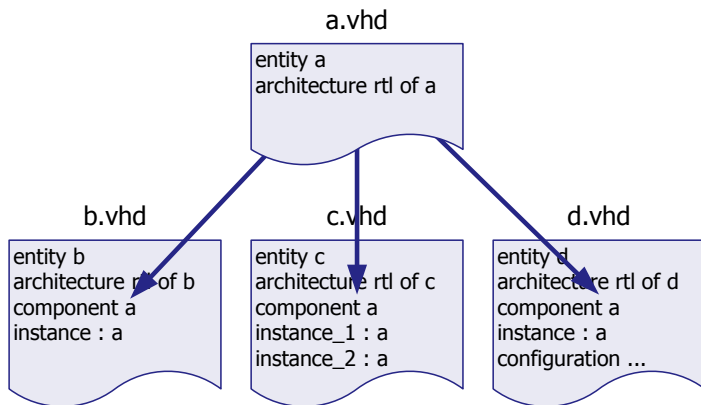

- Entities, architectures, components, instances
- Only one module (entity, architecture) in a single file
- Multiple component declarations are redundant

# Packages

```
package package_name is  
  -- Declaration of  
  -- Types and Subtypes  
  -- Constants, Aliases  
  -- Signals, Files, Attributes  
  -- Functions, Procedures  
  -- Components  
  -- Definition of  
  -- Constants, Attributes  
end package_name;  
  
package body package_name is  
  -- Definition of earlier  
  -- declared Objects  
  -- Functions, Procedures  
  -- Constants  
  -- Declaration/Definition  
  -- of additional Objects  
end package_name;
```

- Place global objects and parameters in packages
- Solves redundancies
- Package holds declarations
- Package body holds definitions
- Include the package with

**use work.package\_name.all;**

# Libraries

- A library contains design units
  - Entities, architectures
  - Packages and package bodies
  - Configurations
- Mapped to a physical path
  - work  $\Rightarrow$  ./work
  - ieee  $\Rightarrow$  \$MODEL\_TECH/./ieee
- Tools place all design units in library work by default
- Libraries work and std are visible by default
- Include other libraries with

```
library library_name ;
```

# Flexible Interfaces

- Problem of large designs
  - Entities have many ports, confusing, difficult naming
  - Redundant interface description (entity, component, instance)
  - Modifying an interface is cumbersome and error-prone
- Solution: Define complex signal records
- Record aggregates wires of an interface

```
type clk_type is
  record
    clk      : std_logic ;
    clkn     : std_logic ;
    clk_2x   : std_logic ;
    clk_90   : std_logic ;
    clk_270  : std_logic ;
  end record;
```

```
-- Create and buffer clocks
entity clk_gen is
  port (
    clk_pad : in  std_logic ;
    clk     : out clk_type );
end clk_gen;
```

# Flexible Interfaces – In and Out

- Split interface in input and output records
- Declare name\_in\_type and name\_out\_type

```
type mem_in_type is  
  record  
    data : mem_data_type;  
  end record;  
  
type mem_out_type is  
  record  
    address      : mem_address_type;  
    data         : mem_data_type;  
    drive_datan  : std_logic ;  
    csn          : std_logic ;  
    oen         : std_logic ;  
    writen      : std_logic ;  
  end record;
```


```
-- Memory controller  
entity mem_ctrl is  
  port (  
    clk      : in   clk_type ;  
    reset   : in   reset_type ;  
    memo    : out mem_out_type;  
    memi    : in   mem_in_type  
    -- Other signals  
    -- Control and data wires  
  );  
end mem_ctrl;
```

```

entity top is
  port (
    data      : inout mem_data_type;
    address   : out  mem_address_type;
    csn       : out  std_logic ;
    oen       : out  std_logic ;
    writen    : out  std_logic
    -- other signals
  );
end top;

```

 - Pads of a chip are often bidirectional
- Infer tristate buffers in top entity
- Do not use inout records
- Strictly avoid bidirectional on-chip wires/buses



# Flexible Interfaces – Inout Implementation

## Memory Controller

```
-- instantiate memory controller
mem_ctrl_i: mem_ctrl
  port map (
    clk    => clk,
    reset  => reset,
    memo  => memo,
    memi  => memi);

-- drive data out
data <= memo.data when memo.driven = '0' else (others => 'Z');
-- read data in
memi.data <= data;
```

- Use the 'Z' value of std\_logic to describe tri-state buffers

## Design Strategies

- Aggregate signals belonging to a logical interface
  - System bus
  - Control and status
  - Receive
  - Transmit
- Use hierarchical records to aggregate multiple interfaces
- Do not place clock and reset into records
- Do not use records for top entity

## Advantages

- Reduces the number of signals
- Simplifies adding and removing of interface signals
- Simplifies route-through of interfaces
- Raises the abstraction level, Improves maintainability

# Customizable VHDL Designs

## What's this?


- VHDL Design is made configurable by parameters
- Modifies its structure, functionality, or behavior
- Facilitates design reuse
- Flexibility

## VHDL gives you

- Entity Signals
- Entity Generics
- Package Constants
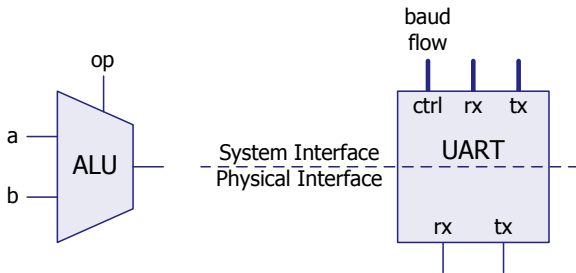
# Control Signals

- Entity contains additional control signals
- Locally to module
- Customization at runtime
- Consumes additional hardware



# Generics

- Entity contains parameters, Locally to module
- Customization at design (compile) time
- Consumes no additional hardware
- Unused logic will be removed

```
entity adder is
  generic (
    n : integer := 4);
  port (
    a, b : in  std_logic_vector (n-1 downto 0);
    ci   : in  std_logic ;
    s    : out std_logic_vector (n-1 downto 0);
    co   : out std_logic );
end adder;
```

# Constants

- Define constants in a package
- Visible for all design units using the package
- Global parameters
- Be careful with naming, Use upper case

```
constant MEM_ADDRESS_WIDTH : integer := 16;
```

```
constant MEM_DATA_WIDTH : integer := 8;
```

```
subtype mem_address_type is
```


```
    std_logic_vector (MEM_ADDRESS_WIDTH-1 downto 0);
```

```
subtype mem_data_type is
```

```
    std_logic_vector (MEM_DATA_WIDTH-1 downto 0);
```
 
# Hierarchical Customization

- Reducing the number of global constants
- Structuring the parameters in configuration records
- Aggregate configurations hierarchically
- Simple and flexible selection of configurations



```
type mem_config_type is  
  record  
    address_width, data_width, banks    : integer ;  
    read_wait_states , write_wait_states : integer ;  
  end record ;  
  
type config_type is  
  record  
    mem : mem_config_type; target : target_config_type ;  
  end record ;  
  
constant MEM_SMALL_FAST : mem_config_type := (  
  address_width => 16, data_width => 8, banks => 1,  
  read_wait_states => 0, write_wait_states => 1);  
  
constant MEM_LARGE_SLOW : mem_config_type := (  
  address_width => 20, data_width => 32, banks => 4,  
  read_wait_states => 4, write_wait_states => 4);  
  
constant MY_SYSTEM : config_type := (  
  mem => MEM_LARGE_SLOW, target => VIRTEX);
```

# Generate Statement

## Generic Adder

```
begin  -- struct

c(0) <= ci; co <= c(n);

fa_for : for i in 0 to n-1 generate
  fa_1 : full_adder
    port map (
      a => a(i),
      b => b(i),
      ci => c(i),
      s => s(i),
      co => c(i+1));
  end generate fa_for ;

end struct ;
```

- Use generate for structural composition
- Applicable for components, processes and parallel statements
- “For”-generate
- “If”-generate but no “else”

# Loops Instead of Generate

## Generic Adder

```
add : process (a, b, ci)
  variable sv : std_logic_vector (n-1 downto 0);
  variable cv : std_logic_vector (n downto 0);
begin -- process add

  cv(0) := ci;

  for i in 0 to n-1 loop
    full_add (a(i), b(i), cv(i), sv(i), cv(i+1));
  end loop; -- i

  s <= sv;
  co <= cv(n);

end process add;
```

- Use loops for generic designs
- Inside processes
- Much simpler than generate statement
- Loop range must be known at compile time

# If-Then-Else Instead of Generate

```
if CALIBRATE then  
  -- remove this logic when  
  -- CALIBRATE = false  
  v.period_counter := r.period_counter + 1;  
  if rising then  
    v.period := v.period_counter;  
    v.period_counter := 0;  
  end if;  
else  
  -- remove this logic when  
  -- CALIBRATE = true  
  v.period := CLK_RATE / FREQUENCY;  
end if;
```

- If-Then-Else is much simpler than generate
- Inside processes
- Unused logic is removed
- CALIBRATE must be known at compile time