

# VHDL Recapitulation

Henning Puttnies

University of Rostock  
Institute of Applied Microelectronics and Computer Engineering

October 12, 2015

# Outline

- 1 Hardware Description Languages
- 2 Abstraction Levels
- 3 A First Example
- 4 Data Types
- 5 Registers and Combinational Logic
- 6 Structural Description
- 7 Additional Information

# Outline

- 1 Hardware Description Languages
- 2 Abstraction Levels
- 3 A First Example
- 4 Data Types
- 5 Registers and Combinational Logic
- 6 Structural Description
- 7 Additional Information


# What are HDLs?

- Modeling language for electronic designs and systems
- VHDL, Verilog
- PALASM, ABEL
- Net list languages such as EDIF, XNF
- Test languages such as e, Vera
- SystemC for hardware/software co-design and verification

# HDL for ...

- Formal description of hardware
- Specification on all abstraction layers
- Simulation of designs and whole systems
- Design entry for synthesis
- Standard interface between CAD tools
- Design reuse

# Design methodology

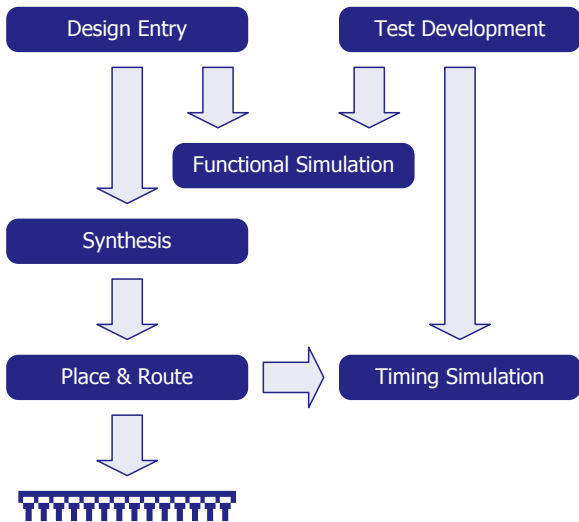

# Pros and Cons of HDLs

## Pros

- Speeds up the whole design process
- Powerful tools
- Acts as an interface between tools
- Standardized
- Design reuse


## Cons

- Learning curve
- Limited support for target architecture

# Outline

- 1 Hardware Description Languages
- 2 Abstraction Levels**
- 3 A First Example
- 4 Data Types
- 5 Registers and Combinational Logic
- 6 Structural Description
- 7 Additional Information

# Design Abstraction Levels

 


**Behavior** Sequential statements, implicit registers

**Data flow** Register transfer level (RTL), Parallel statements, explicit registers

**Structure** Design hierarchy, Wiring components

# HDL Abstraction Levels

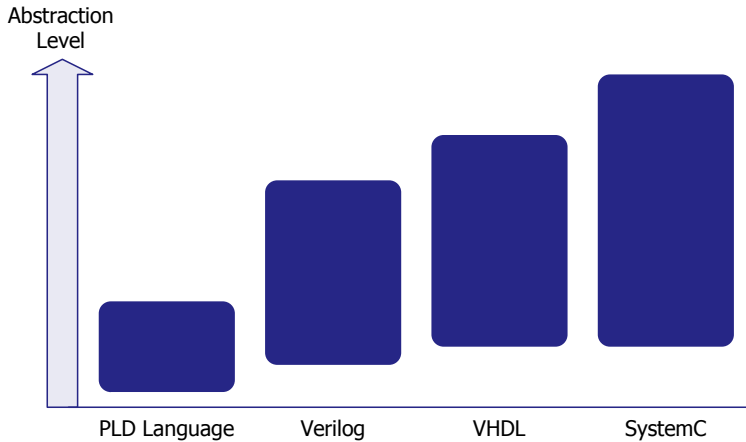


# Outline

- 1 Hardware Description Languages
- 2 Abstraction Levels
- 3 A First Example**
- 4 Data Types
- 5 Registers and Combinational Logic
- 6 Structural Description
- 7 Additional Information

# A First Example
 
## Multiplexer

```
library ieee ;  
use ieee . std_logic_1164 . all ;  
  
entity mux is  
  port (  
    a, b : in   std_logic_vector (3 downto 0);  
    s    : in   std_logic ;  
    o    : out  std_logic_vector (3 downto 0));  
end mux;  
  
architecture behavior of mux is  
begin -- behavior  
  o <= a when s = '0' else b;  
end behavior;
```



# Library

```
library ieee ;  
use ieee . std_logic_1164 . all ;
```

- Makes library ieee visible
- Use objects within the library
- Use package std\_logic\_1164
- Makes std\_logic and std\_logic\_vector visible

# Entity

```
entity mux is  
  port (  
    a, b : in   std_logic_vector (3 downto 0);  
    s   : in   std_logic ;  
    o   : out  std_logic_vector (3 downto 0));  
end mux;
```

- Defines the name of the module
- Describes the interface
  - Name of the ports
  - Direction
  - Type

# Architecture

```
architecture behavior of mux is  
begin -- behavior  
    o <= a when s = '0' else b;  
end behavior;
```

- Implements the module
  - Behavior
  - Structure
  - RTL description
- Entity and architecture are linked by name (mux)
- Name of architecture (behavior)
- More than one architecture per entity allowed

# Outline

- 1 Hardware Description Languages
- 2 Abstraction Levels
- 3 A First Example
- 4 Data Types**
- 5 Registers and Combinational Logic
- 6 Structural Description
- 7 Additional Information

# Data Types

- Std\_logic:
  - Represents electrical behaviour of circuit nodes
  - Can have 9 different states
- Std\_logic\_vector: array of std\_logic values
- Signed and unsigned
  - Arrays similar to std\_logic\_vector
  - Main difference: arithmetic operators like  $+$   $-$   $*$  are defined
- Types like integer and natural often used with "range"
- No floating point types

logic vlaue		logic state		
		low	unknown	high
uninitialized		U		
strength	strong	0	X	1
	weak	L	W	H
	high-impedance	Z	Z	Z
don't care		-		

# Outline

- 1 Hardware Description Languages
- 2 Abstraction Levels
- 3 A First Example
- 4 Data Types
- 5 Registers and Combinational Logic**
- 6 Structural Description
- 7 Additional Information


# Register

```
entity reg is
  port (
    d, clk : in  std_logic ;
    q      : out std_logic );
end reg;

architecture rtl of reg is
begin  -- rtl

  reg: process (clk)
  begin  -- process reg
    if rising_edge (clk) then
      q <= d;
    end if ;
  end process reg;

end rtl ;
```

 


- Sensitivity list only contains the clock
- Assignment on the rising edge of the clock
- Not transparent

# Parallel Processing
 
## Half Adder

```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity half_adder is  
  port (  
    a, b : in  std_logic;  
    s, co : out std_logic);  
end half_adder;  
  
architecture rtl of half_adder is  
begin -- rtl  
  s <= a xor b;  
  co <= a and b;  
end rtl;
```



- Implicit gates
- Signals are used to wire gates
- Computes signals  $s$  and  $co$  from  $a$  and  $b$  in **parallel**


## Full Adder

```

entity full_adder is
  port (
    a, b, ci : in  std_logic ;
    s, co   : out std_logic );
end full_adder ;

architecture beh_par of full_adder is
  signal s1, s2, c1, c2 : std_logic ;
begin
  -- behavior
  -- half adder 1
  s1 <= a xor b;
  c1 <= a and b;
  -- half adder 2
  s2 <= s1 xor ci;
  c2 <= s1 and ci;
  -- evaluate s and co
  s <= s2;
  co <= c1 or c2;
end beh_par;

```

 

- All statements are processed in **parallel**
- A signal **must not** be driven at two places
- Order of statements is irrelevant

# Sequential Processing – Processes

```
architecture beh_seq of full_adder is
begin  -- beh_seq

    add: process (a, b, ci)
        variable s_tmp, c_tmp : std_logic ;
    begin  -- process add
        -- half adder 1
        s_tmp := a xor b;
        c_tmp := a and b;
        -- half adder 2
        c_tmp := c_tmp or (s_tmp and ci);
        s_tmp := s_tmp xor ci;
        -- drive signals
        s <= s_tmp;
        co <= c_tmp;
    end process add;

end beh_seq;
```

- All statements are processed sequential
- Sensitivity list (a, b, ci)
- Multiple variable assignments are allowed
- Order of statements is relevant
- Variables are updated immediately
- Signals are updated at the end of a process
- Try to avoid multiple signal assignments

# Parallel versus Sequential Processing


```
p1: process (a, b)
begin  -- process p1
      -- sequential statements
      -- ...
      -- drive process outputs
      x <= ...
end process p1;

p2: process (c, x)
begin  -- process p2
      -- sequential statements
      -- ...
      -- drive process outputs
      y <= ...
end process p2;

-- drive module outputs
o <= x or y;
```

- process p1, process p2 and o are processed in parallel
- Statements within processes are sequential
- Inter-process communication with signals
- Signal values are evaluated recursively in zero time
- Simulator uses delta cycles

# Real time and delta cycles

 

# Signals and Variables

## Signals

- Inside and outside processes
- Communication between parallel statements and processes
- Only the last assignment within a process is evaluated
- Signal is updated at the end of a process
- Signals are wires

## Variables


- Inside processes only
- For intermediate results
- Multiple assignments allowed
- Immediate update

# Outline

- 1 Hardware Description Languages
- 2 Abstraction Levels
- 3 A First Example
- 4 Data Types
- 5 Registers and Combinational Logic
- 6 Structural Description**
- 7 Additional Information
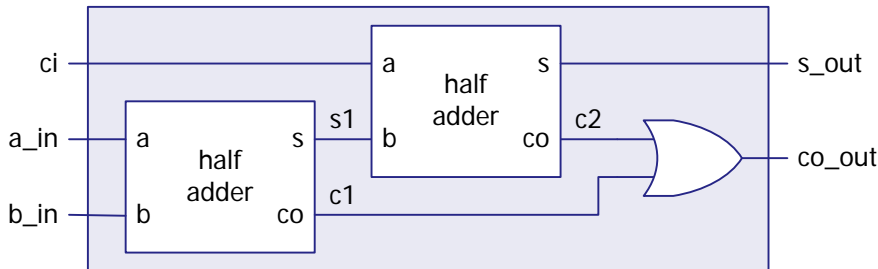
# Structural Description

- Module composition
- Wiring of Modules
- Design Hierarchy
- “Divide and conquer”



```
architecture structural of full_adder is
  component half_adder
    port (
      a, b : in  std_logic ;
      s, co : out std_logic );
  end component;
  signal s1, c1, c2 : std_logic ;
begin -- structural
  half_adder_1 : half_adder
    port map (
      a => a_in, b => b_in,
      s => s1, co => c1);

  half_adder_2 : half_adder
    port map (
      a => ci, b => s1,
      s => s_out, co => c2);

  co_out <= c1 or c2;

end structural ;
```

- Make module half\_adder known with component declaration
- Module instantiation
- Connect ports and signals

# Outline

- 1 Hardware Description Languages
- 2 Abstraction Levels
- 3 A First Example
- 4 Data Types
- 5 Registers and Combinational Logic
- 6 Structural Description
- 7 Additional Information**

## Additional Information

### Syntax Reference

- Vivado VHDL templates: Project Manager → Templates
- Wikibooks: <https://de.wikibooks.org/wiki/VHDL-Tutorium>

### Literature

- Hubert Keaslin: Digital Integrated Circuit Design - From VLSI Architecture to CMOS Fabrication
- Paul Molitor, Jörg Ritter: Kompaktkurs VHDL